

Topic 8


Counters

Counters

- A digital circuit that counts in different format: binary, decimal, one-hot, signed, unsigned...
- An n -bit binary counter can count up to numbers
- An n -bit binary counter consists of flip-flops
- Count up or count down, increment or decrement once per clock cycle – counting number of clock cycles
- Counters:
 - Asynchronous counters
 - Synchronous counters

Synchronous Binary Counter

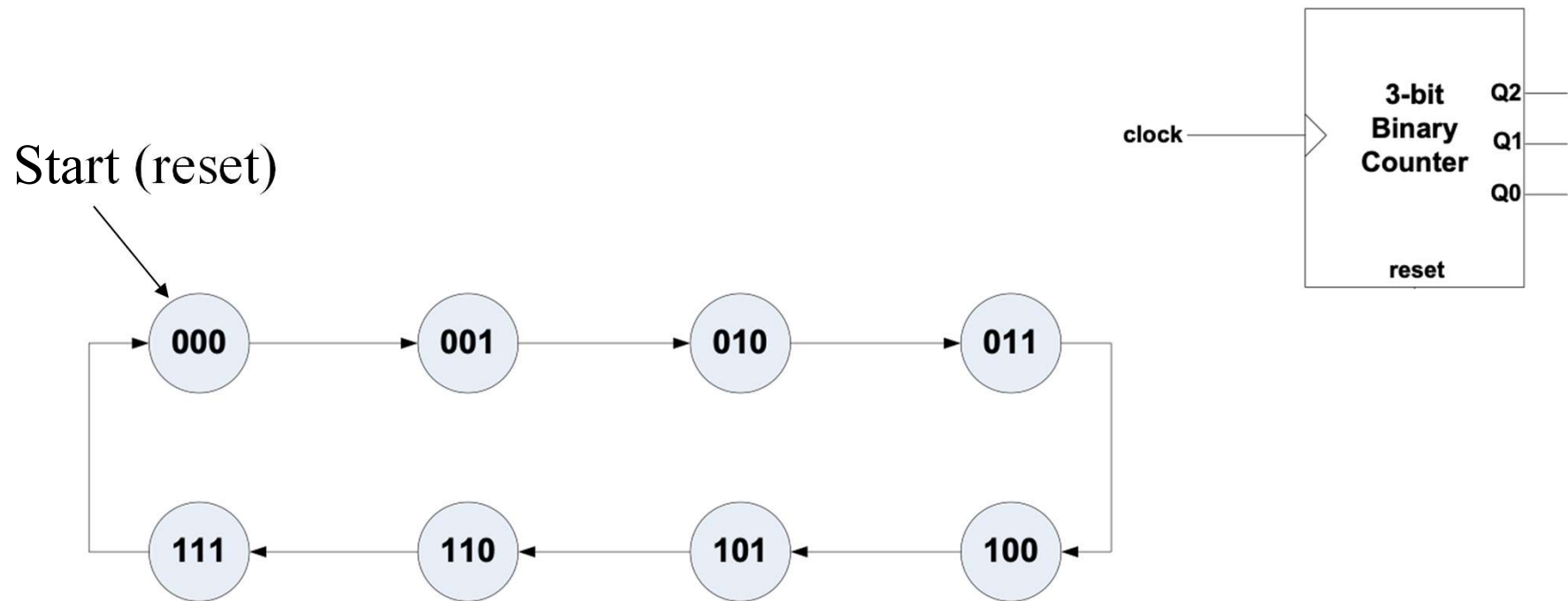- All the flip-flops are triggered by (synchronized to) the same — synchronous counter
- May be implemented by different type of flip-flops
- Example: a 3-bit binary counter can count through this sequence



Synchronous Binary Counter Design

- Following the counting sequence

Current Value (state)			Next Value (state)		
Q2	Q1	Q0	Q2 ⁺	Q1 ⁺	Q0 ⁺
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Counter Implemented with D Flip-Flop

- Use D flip flops to hold values: $Q^+ =$

Present State			Next State			D flip flop input		
Q2	Q1	Q0	Q2 ⁺	Q1 ⁺	Q0 ⁺	D2	D1	D0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	0
1	0	0	1	0	1	1	0	1
1	0	1	1	1	0	1	1	0
1	1	0	1	1	1	1	1	1
1	1	1	0	0	0	0	0	0


Same

Counter Implemented with D Flip-Flop

- Drop the columns for Q^+

Present State (D-FF outputs)			Next State (D-FF inputs)		
Q2	Q1	Q0	D2	D1	D0
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Truth table inputs Truth table outputs

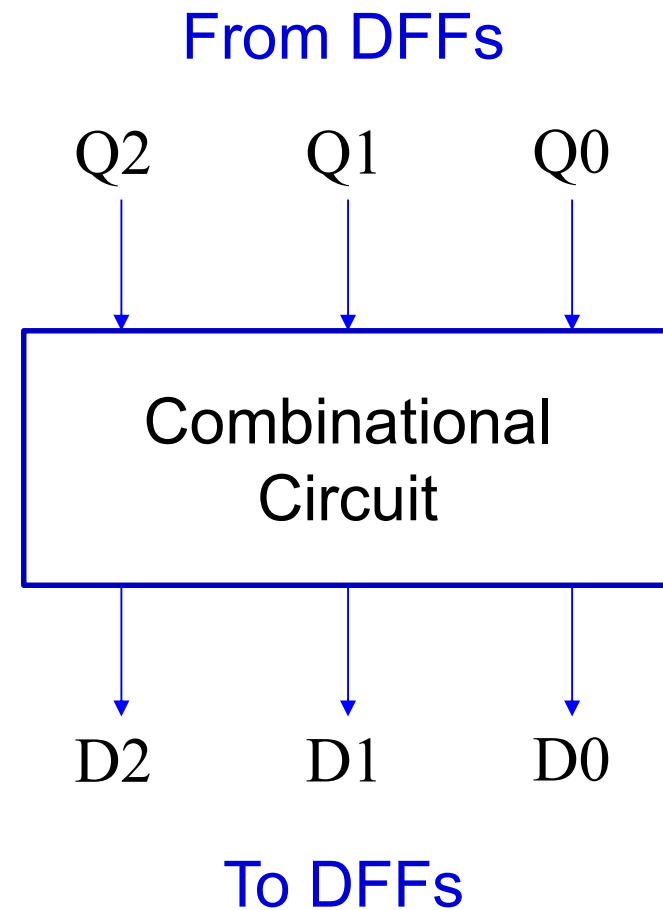

State Registers Implemented with D Flip-Flop

D2

Q2 \ Q1Q0	00	01	11	10
0	0	0	1	0
1	1	1	0	1

D2 =

D1

Q2 \ Q1Q0	00	01	11	10
0	0	1	0	1
1	0	1	0	1

D1 =

D0

Q2 \ Q1Q0	00	01	11	10
0	1	0	0	1
1	1	0	0	1

D0 =


- The input equation can be generalized as

Dn =

Present State			D flip flop input		
Q2	Q1	Q0	D2	D1	D0
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0


Synchronous Binary Counter with D Flip-Flop

- 3-bit binary counter by D FF

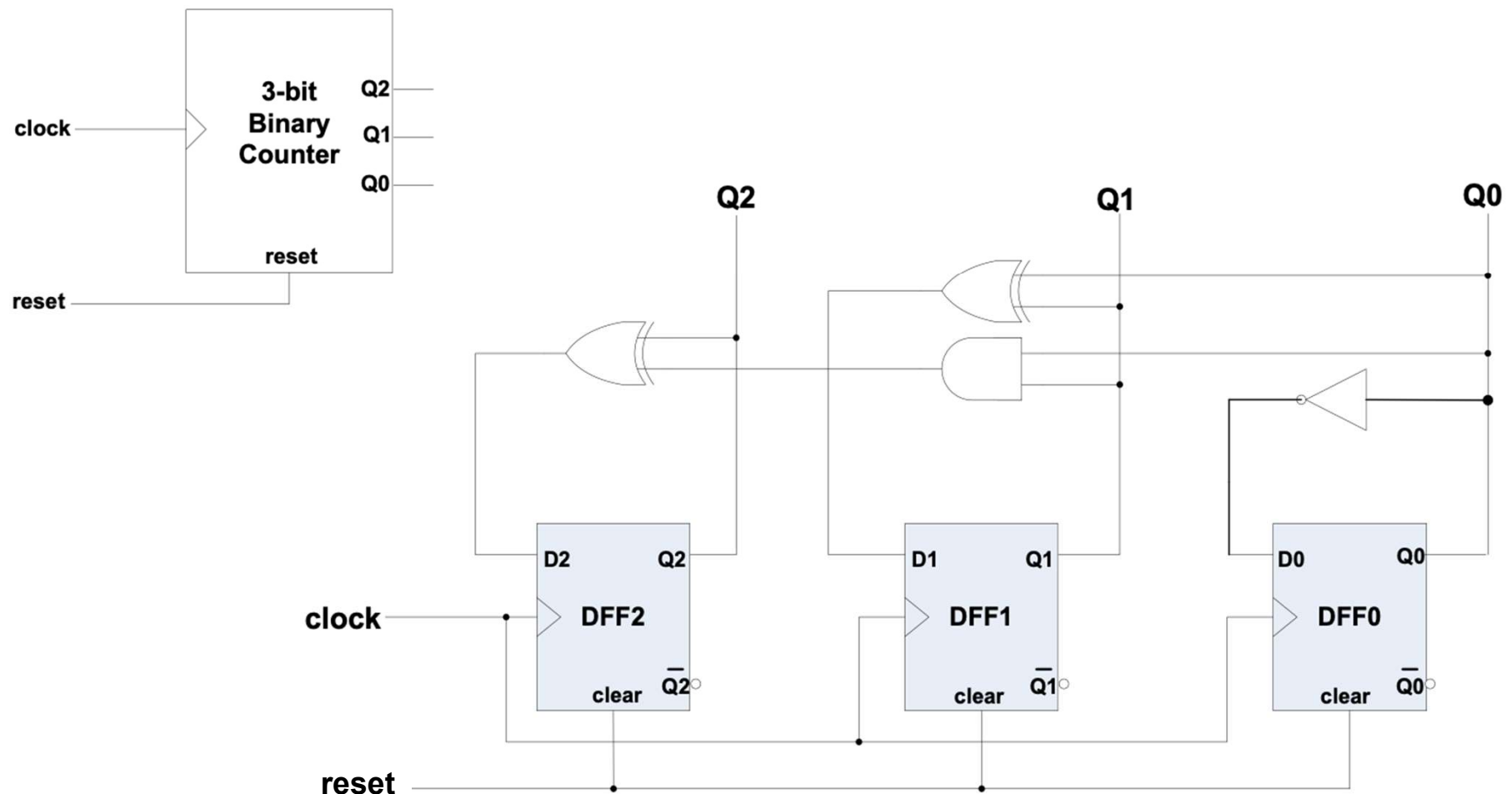


Synchronous Binary Counter with D Flip-Flop

- 3-bit binary counter by D FF

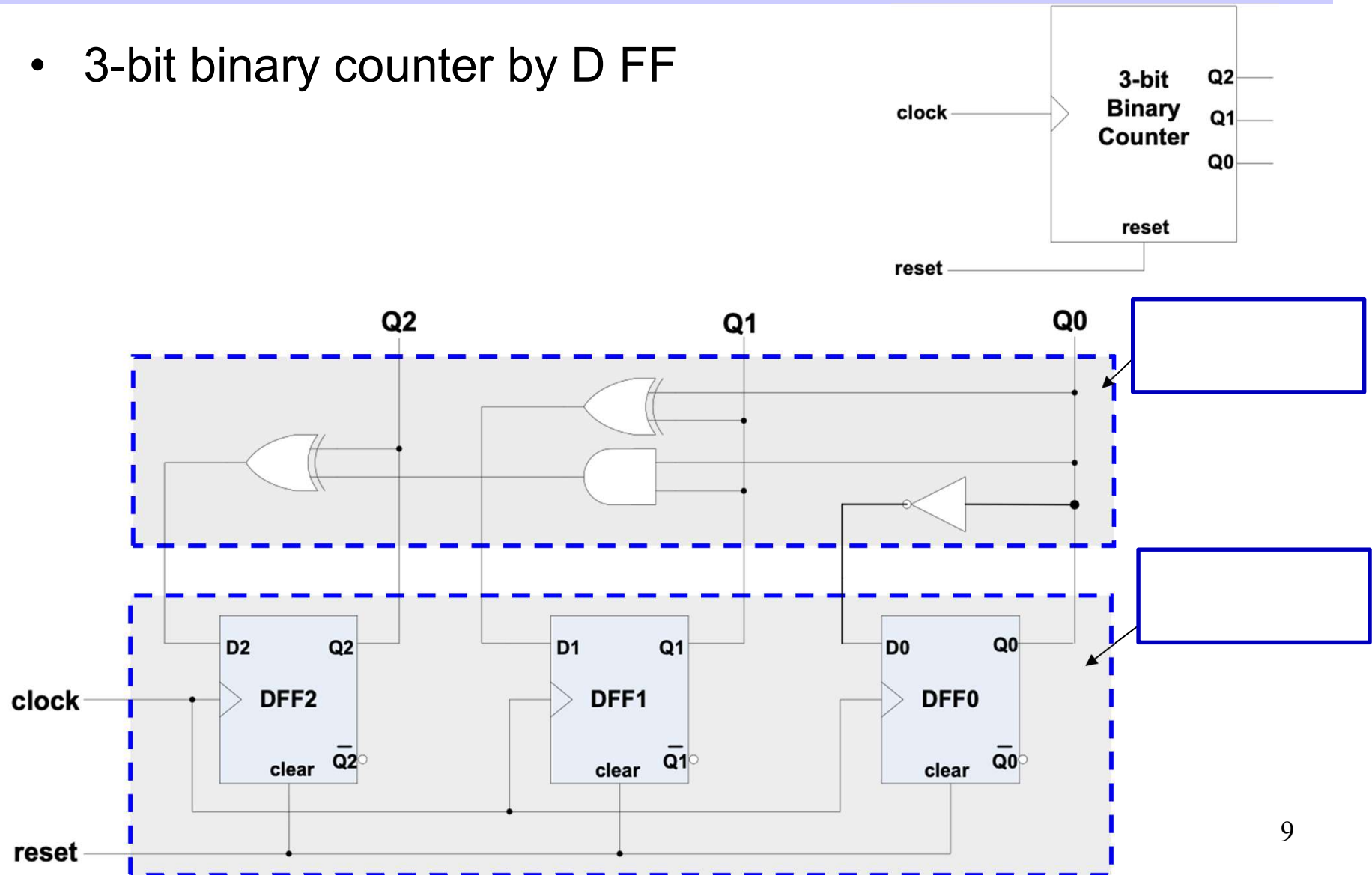


Verilog Model: Synchronous Binary Counter
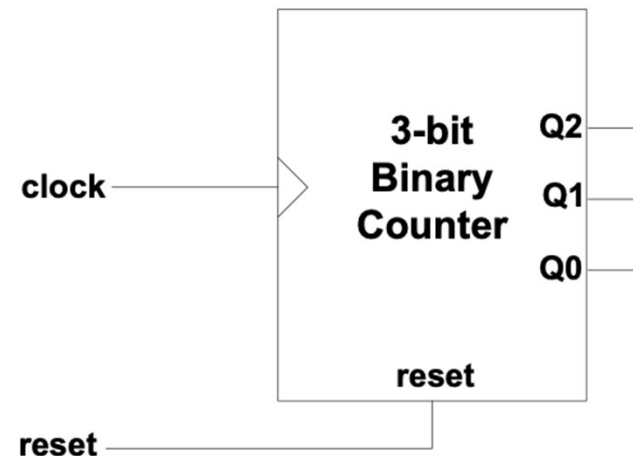
```
module counter_N_bit (clock, reset, Q);  
  parameter N = 3; ← Defines a constant N  
  input      clock, reset;  
  output     [N-1:0] Q;  
  reg        [N-1:0] Q;  
  always @ (posedge reset or posedge clock)  
    if (reset == 1'b1) Q <= 0;  
    else                Q <= Q + 1;  
endmodule
```




Asynchronous Binary Counter – Ripple Counter

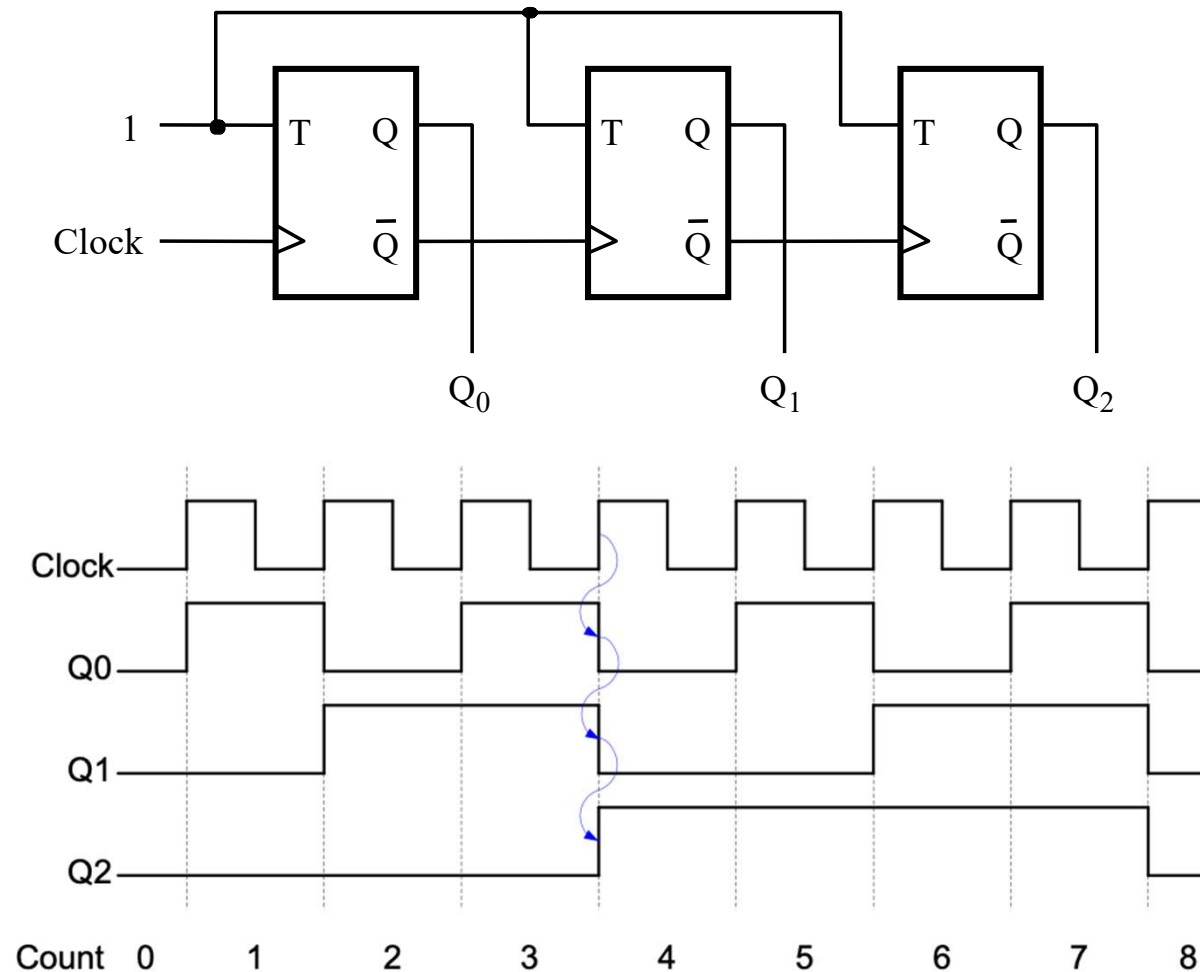- Flip flops are not triggered by a global clock signal
 - Example: up counter with T flip flops




Asynchronous Binary Counter – Ripple Counter

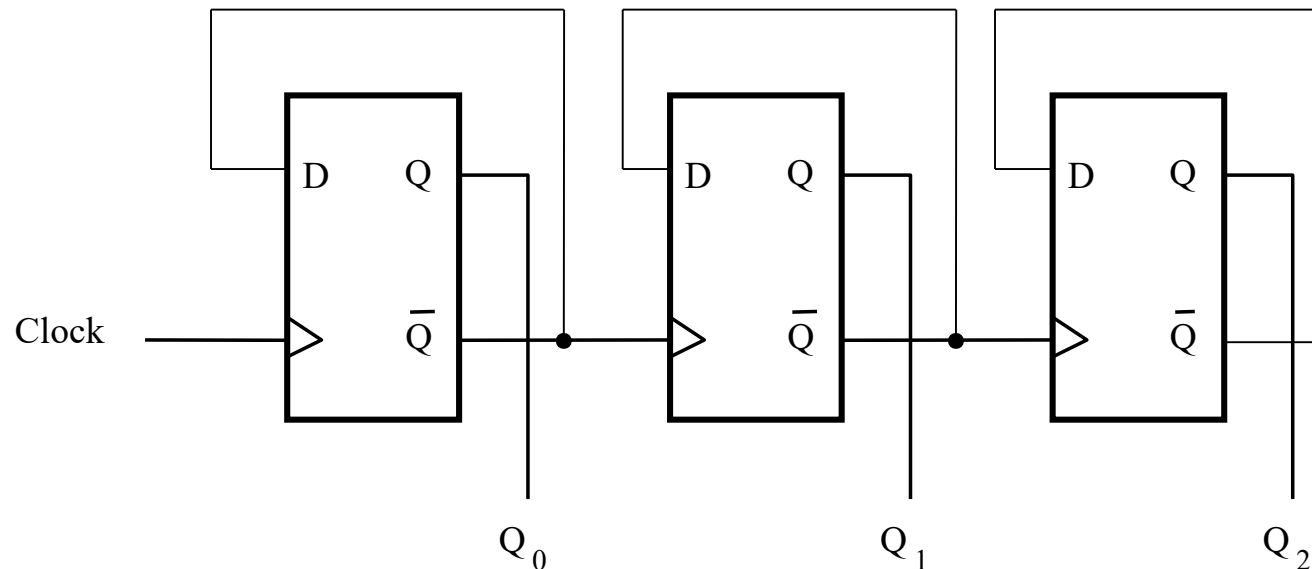- Example:
 - Alternative binary ripple counter, with D flip flops, up counter




Asynchronous Binary Counter – Ripple Counter

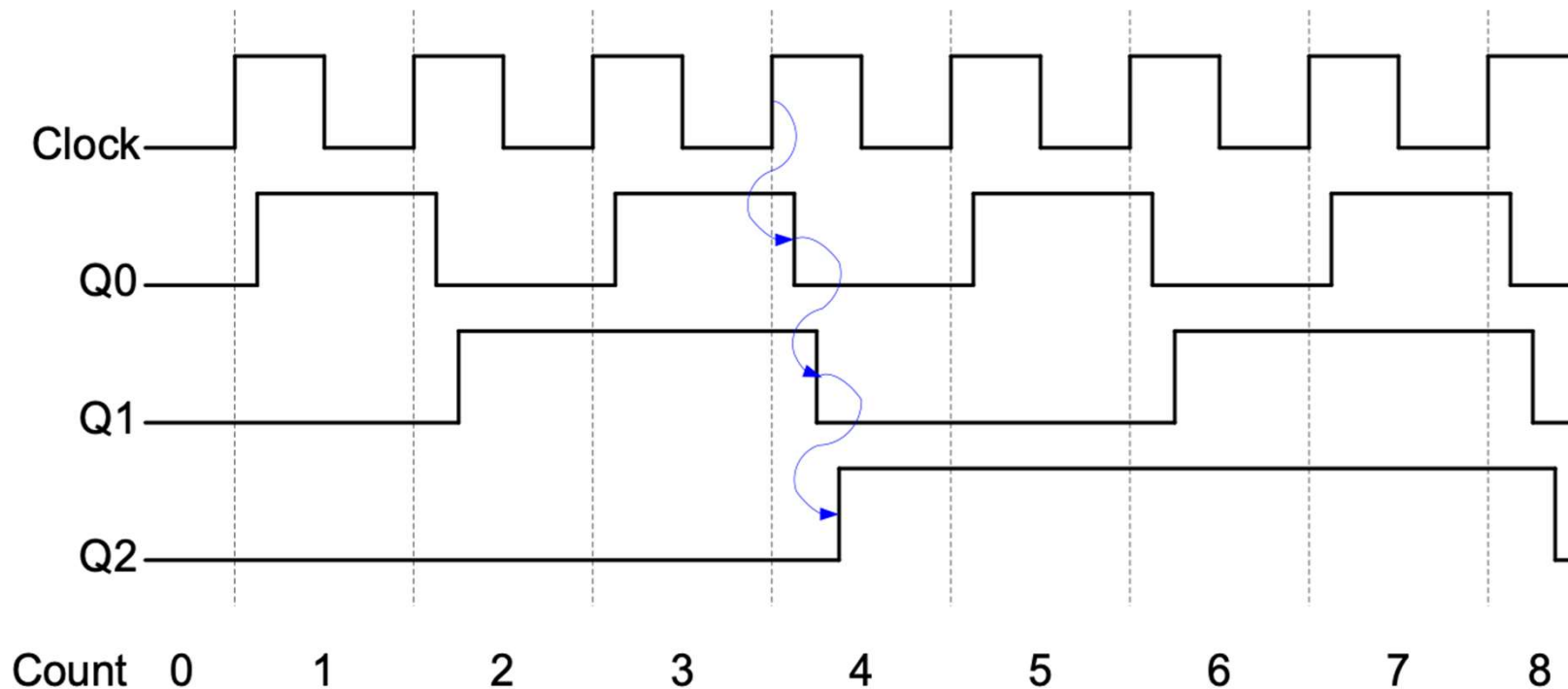- Problem with asynchronous counters:
 - Delays caused by each stage – timing issues



Synchronous Counter with Control Input

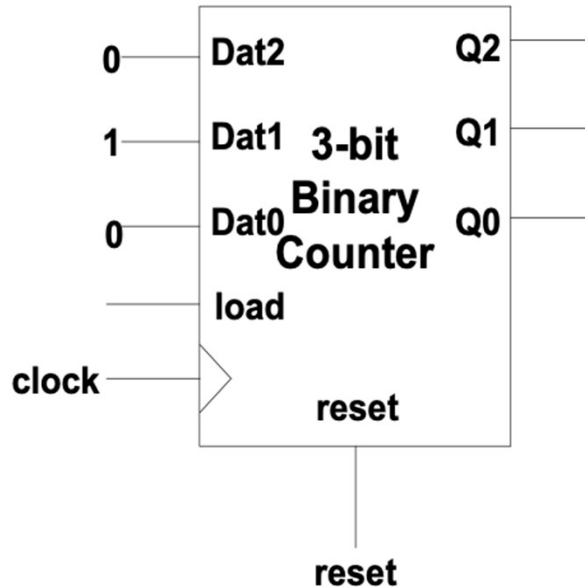- Control inputs may be added to the flip flops in a binary counter to control the behavior of the counter
- Load (Parallel Load):**
 - Numbers can be loaded into the counter anytime when the load input is high, thus the count sequence can be customized






Counting sequence:

010 → ... → 110 → 111 → 000 → 001 ...


Implementation of Parallel Load

- Using for the D inputs of DFFs

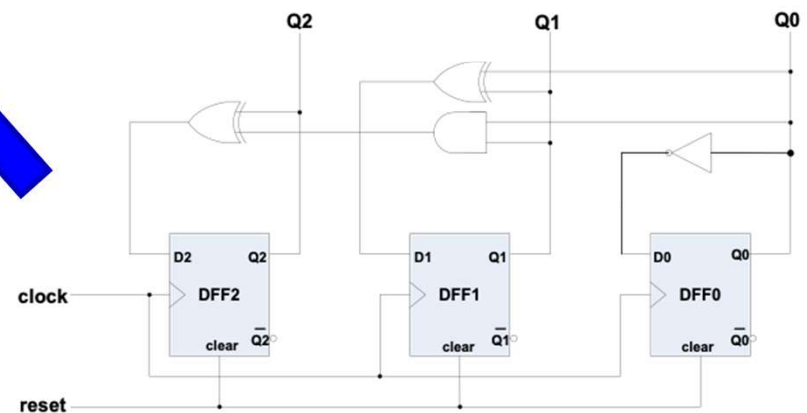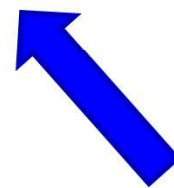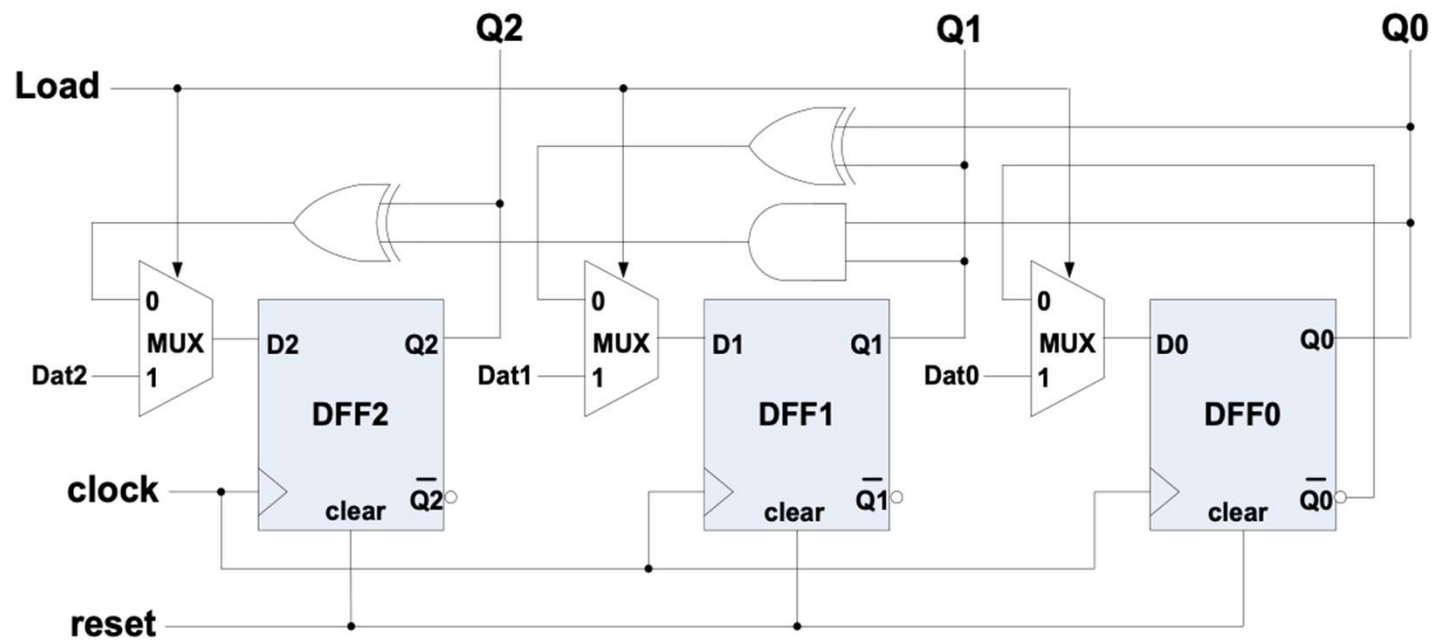


Verilog Model: Counter with Parallel Load
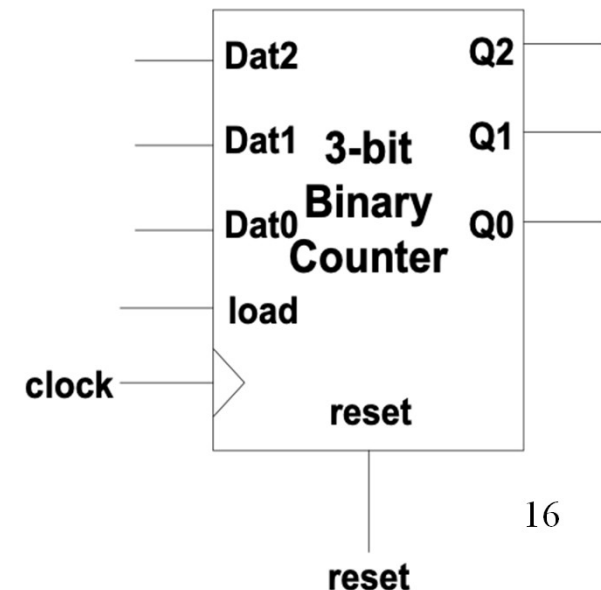
```
module counter_N_bit (clock, reset, load, Dat, Q);  
  parameter N = 3;  
  input      clock, reset, load;  
  input      [N-1:0]    Dat;  
  output     [N-1:0]    Q;  
  reg       [N-1:0]    Q;  
  always @   (posedge reset or posedge clock)  
    if (reset == 1'b1) Q <= 0;  
    else if (load == 1'b1) Q <= Dat;  
    else Q <= Q + 1;  
endmodule
```




Binary Counter with Count Enable

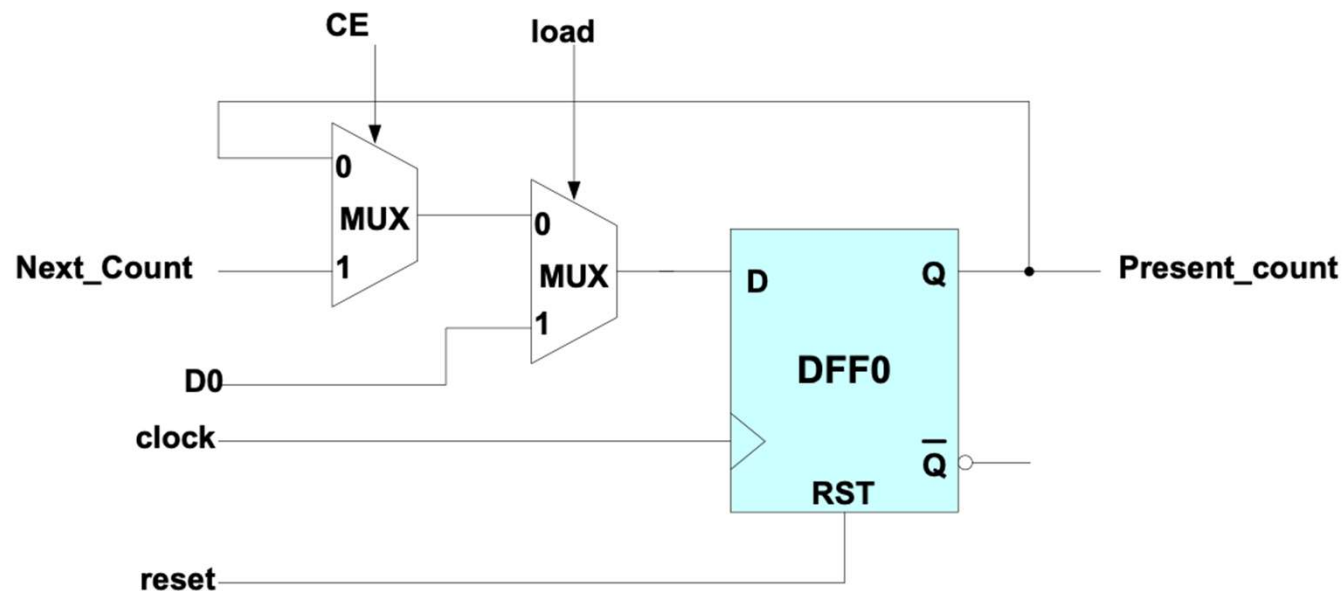- **Count Enable (CE) :**
 - when CE = 1, counter counts
 - when CE = 0, counter holds the values
- Used to hold the counter to
 - Wait certain acknowledge signal coming from other devices
 - Concatenate small counters into bigger ones
- Implementation of 1-bit of a counter with both CE and load:



Binary Counter with CE and Load

- 3-bit binary counter with load and CE

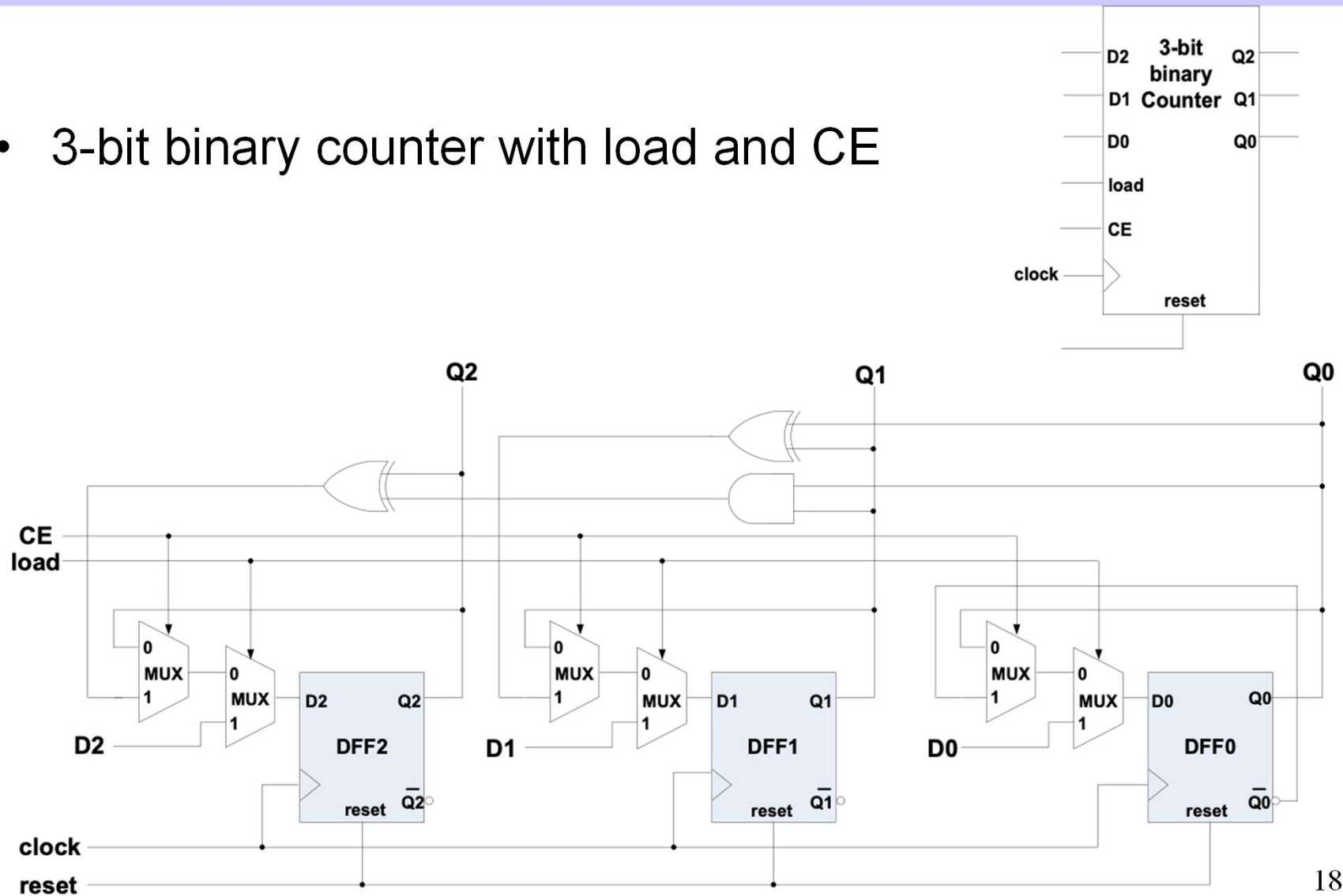

Priority of External Control Signals


- Function table of a counter with external controls
 - a prioritized hierarchical control structure

reset	load	CE	Action on the rising clock edge
1	X	X	Clear ($Q_n \leq 0$)
0	1	X	Load ($Q_n \leq D_n$)
0	0	1	Count
0	0	0	Hold (No Change)

N-bit Binary Counter

- Count Enable Output (CEO)

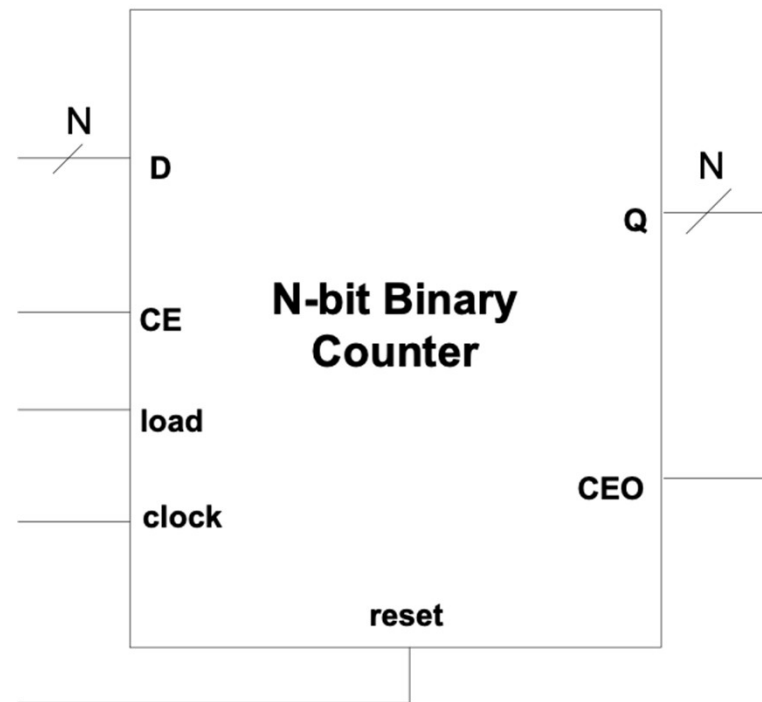
$$\text{CEO} = \text{CE} \cdot Q_{N-1} \cdot Q_{N-2} \cdot \dots \cdot Q_0$$



Verilog Model: Counter with Count Enable

```
module counter_N_bit (clock, reset, load, CE, D, Q, CEO);  
  parameter N = 3;  
  input      clock, reset, load, CE;  
  input      [N-1:0] D;  
  output     [N-1:0] Q;  
  output     CEO;  
  reg        [N-1:0] Q;  
  
  always @ (posedge reset or posedge clock)  
    if (reset == 1'b1) Q <= 0;  
    else if (load == 1'b1) Q <= D;  
    else if (CE == 1'b1) Q <= Q + 1;  
    else Q <= Q;  
  
  assign CEO = CE & (&Q);  
endmodule
```

Executed
concurrently

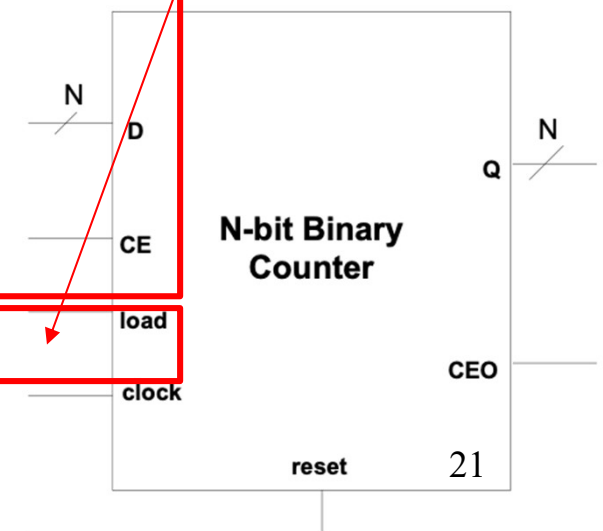

Testbench Written in Verilog

```
module Test_Banch;  
  parameter half_period = 50;  
  parameter counter_size = 4;  
  
  wire [counter_size-1:0] Q;  
  reg [counter_size-1:0] Din;  
  reg clock, load, reset, CE;
```

```
  counter_N_bit #(counter_size) UUT (clock,reset,load,CE,Din,Q,CEO) ;
```


```
  initial begin  
    #0    clock = 0; Din = 0; load = 0; CE = 1; reset = 1;  
    #100  reset = 0;  
    #200  Din = 8; load = 1;  
    #100  load = 0;  
    #300  CE = 0;  
    #200  CE = 1;  
  end
```

```
  always #half_period clock = ~clock;
```


```
  initial #2000 $stop;
```

```
endmodule
```

All executed
concurrently

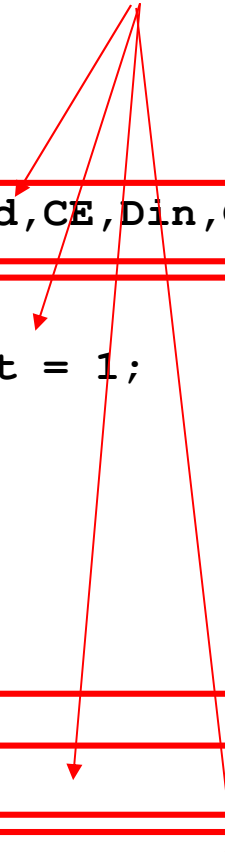


Simulation Result

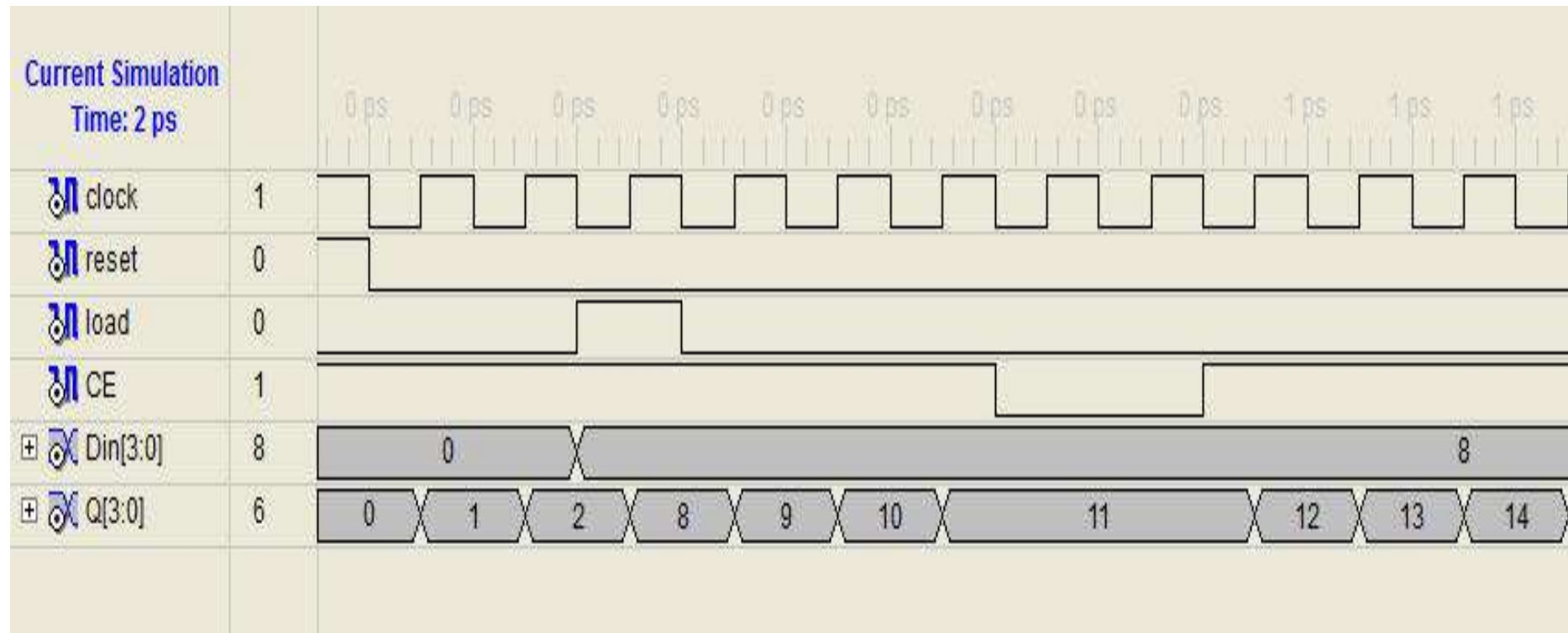

Customize Counting Sequence

- What does this circuit do?

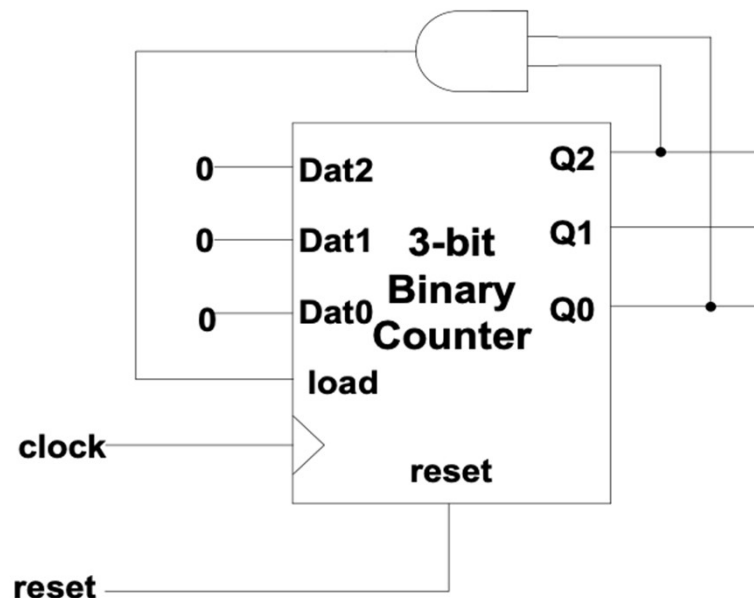


Q2	Q1	Q0	Q2 ⁺	Q1 ⁺	Q0 ⁺
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	0	0	0
1	1	0	X		
1	1	1			

- load = Q2Q0, initial number = 000
- The count sequence now becomes
000 → 001 → ... → 101 → 000
(modulo-6 counter)

Customize Counting Sequence

- What does this do?

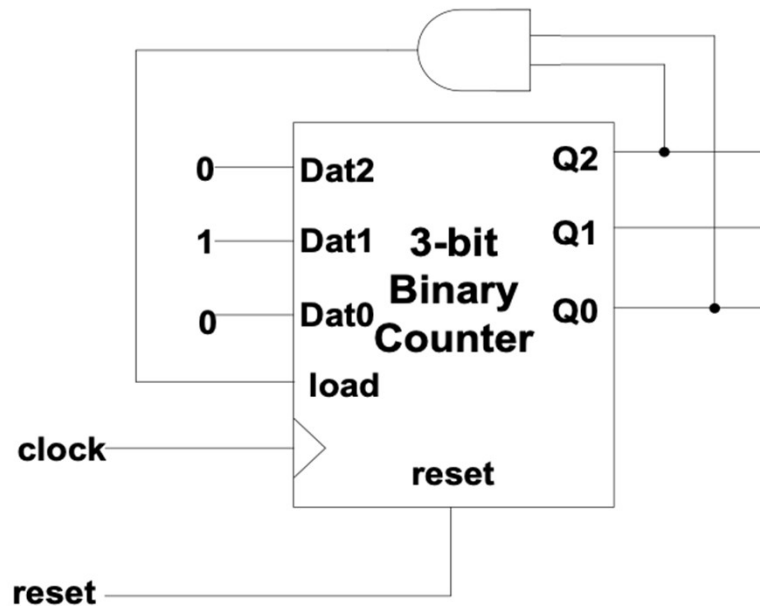

Q2	Q1	Q0	Q2 ⁺	Q1 ⁺	Q0 ⁺
0	0	0	X		
0	0	1			
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	0	1	0
1	1	0	X		
1	1	1			

- load = Q2Q0, initial number = 010
- The count sequence is
 $000 \rightarrow \dots \rightarrow 101 \rightarrow 010 \rightarrow 011 \rightarrow \dots \rightarrow 101 \rightarrow 010 \rightarrow \dots$

$\underbrace{\hspace{10em}}$
In first cycle

An Application of Counter: Clock Divider

- Slows a clock down by reducing its frequency




- Generates slower pulses



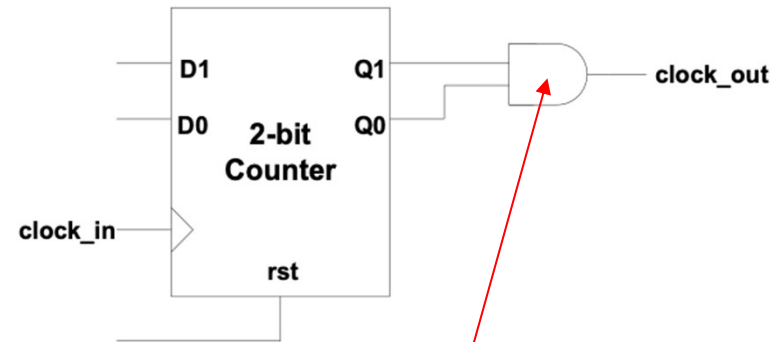
Example: Divide by 4

- 4-fold clock divider: 2-bit binary counter
- The clock_out generates one pulse for every four input clock cycles.
 - So the frequency of the clock_in is reduced by times
- Q1 serves the same purpose with 50% duty cycle



Ideal case, delay ignored


T1 35 T2 75 Tdelta 40

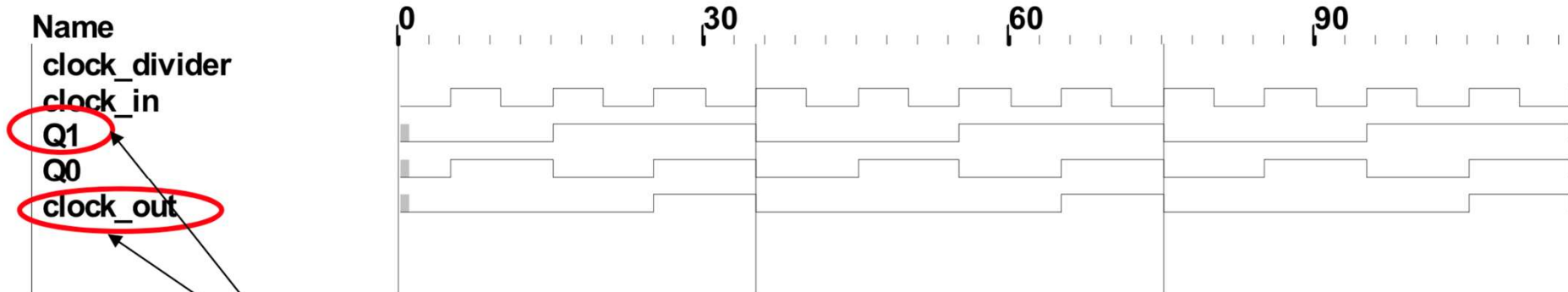

Both have the same slower frequency

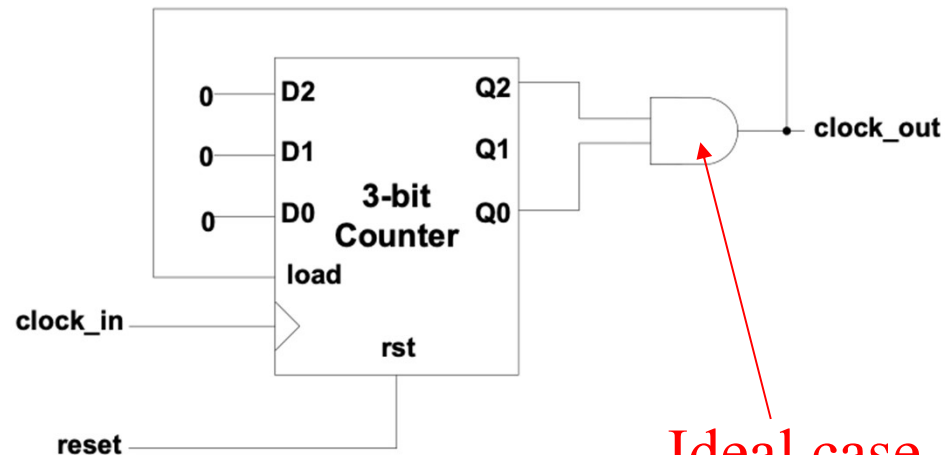Example: Divide by 6


- $2^2 < 6 < 2^3$, at least a 3-bit counter
- Countering sequence: $000 \rightarrow 001 \rightarrow 010 \rightarrow 011 \rightarrow 100 \rightarrow 101 \rightarrow 000$
- The output should be a logic “1” whenever Q2 and Q0 are high
 - $\text{clock_out} = \text{load} = Q2 \ \& \ Q0$



Ideal case, delay ignored

T1 T2 Tdelta

Name
clock_divider
clock_in
clock_out

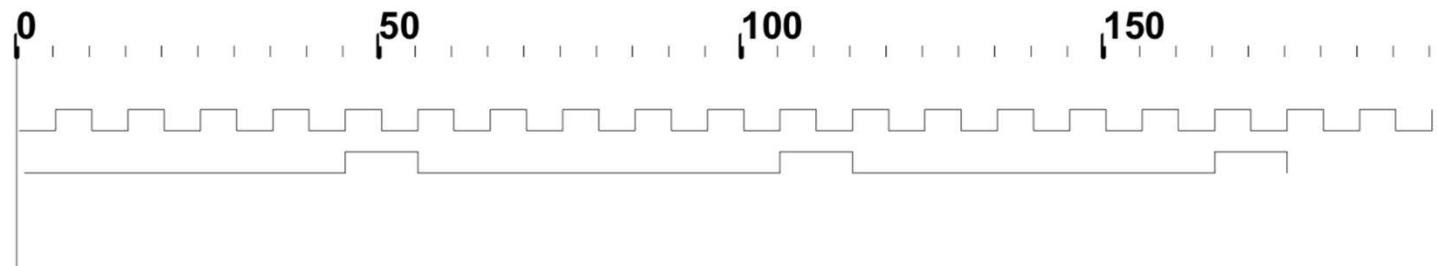


Divide by N

- In general, for N-fold Clock Divider
 - $2^{n-1} < N \leq 2^n$, where n is the size of counter
 - N-1 should be the upper bound of the counter's counting sequence, i.e.
 $0 \rightarrow 1 \rightarrow \dots \rightarrow N-1 \rightarrow 0$
 - Thus the counter should be force back to 0 using load input when it reaches the number N-1
 - If B_{N-1} is the binary equivalent of decimal number N-1, both load and output clock can be formed by ANDing the bits of '1's in B_{N-1}

Gated Clock


- Propagation delay of the output clock:
 - The output of the clock dividers comes from a combinational logic circuit (single AND gate or a net of gates in multiple levels)
 - The output will be delayed due to delay of the gates
 - Amount of delay depends on the combinational circuit
 - This kind of output is called
 - Asynchronous output may cause if the output is used as a synchronizing signal (i.e. clock)
 - **Clock skew:** the difference in the arrival time of clock signal between *two sequentially-adjacent registers* (wikipedia)

Gated Clock

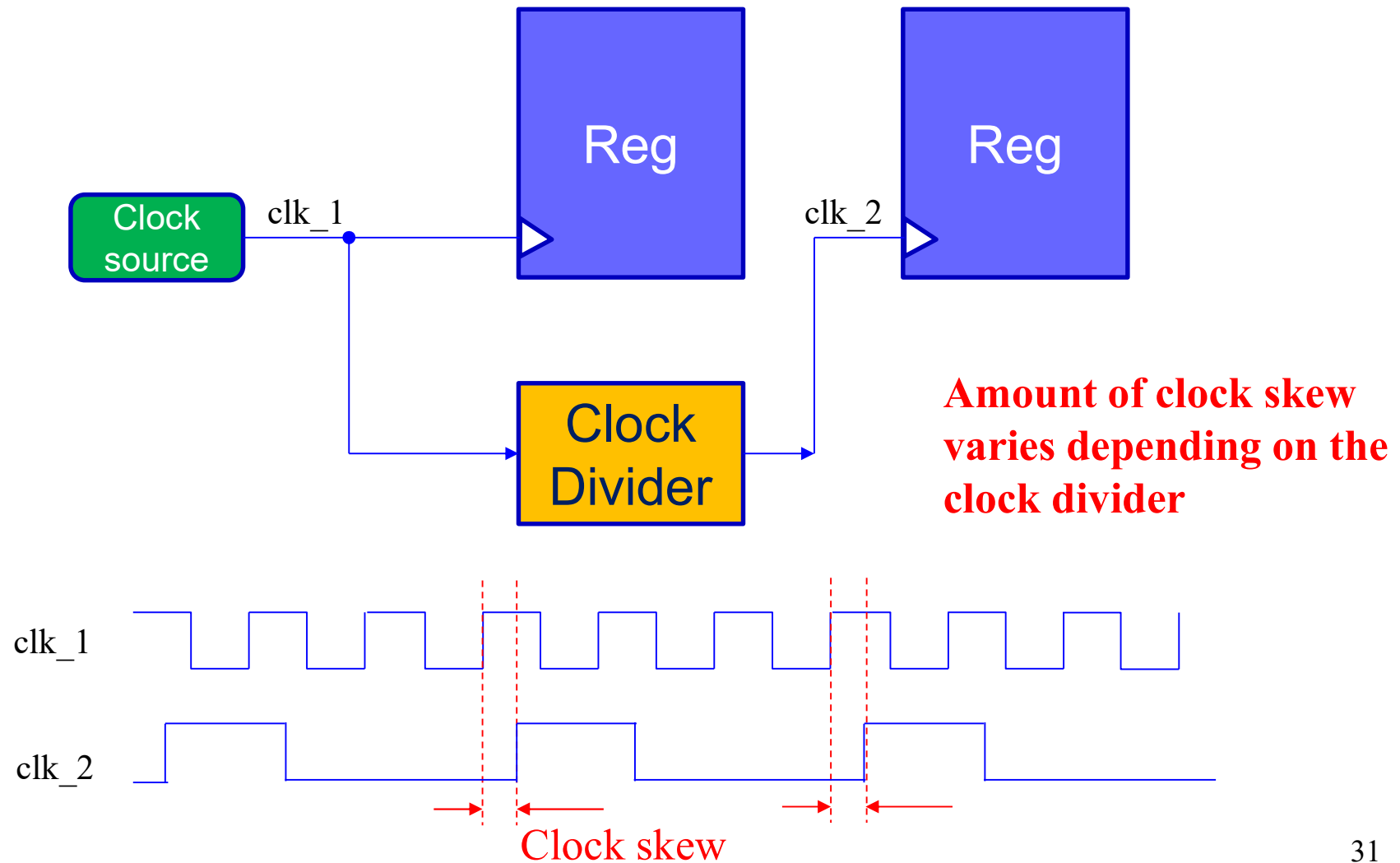



Synchronizer

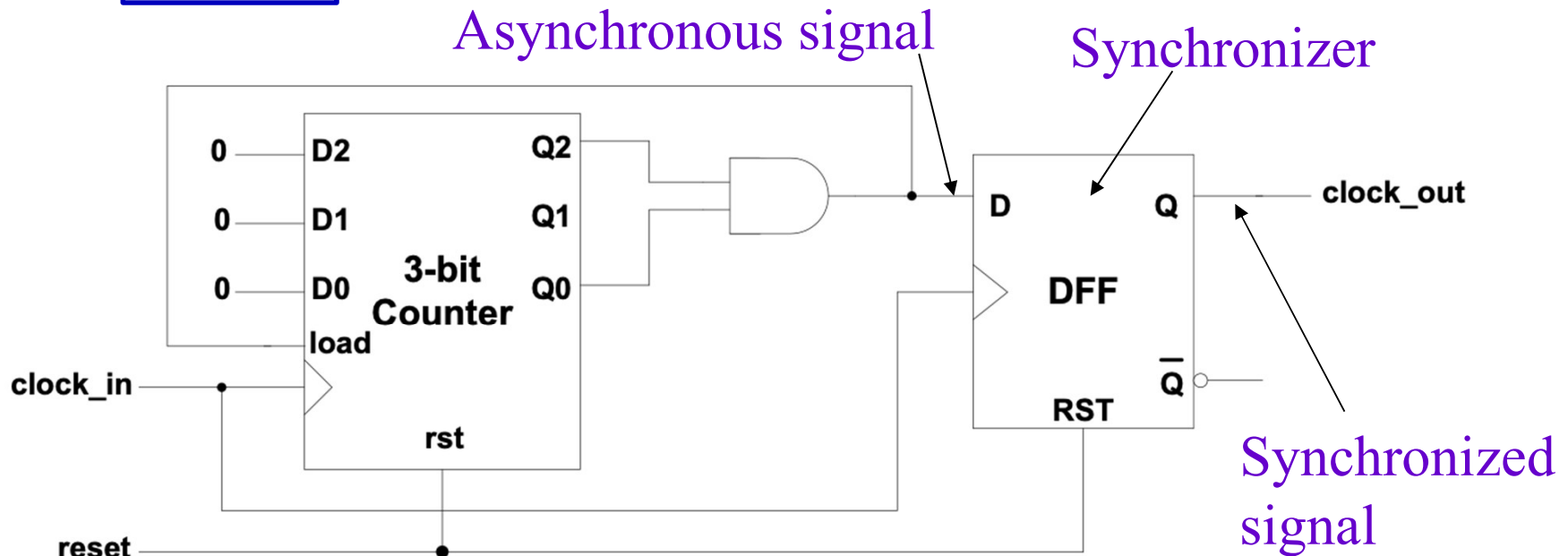- One possible solution to reduce clock skew is to synchronize the output by a




- Synchronizer delays the input asynchronous signal by up to 1 clock cycle
 - But aligns the synchronized signal with clock
 - Clock skew is not completely removed, only reduced

Synchronized Clock

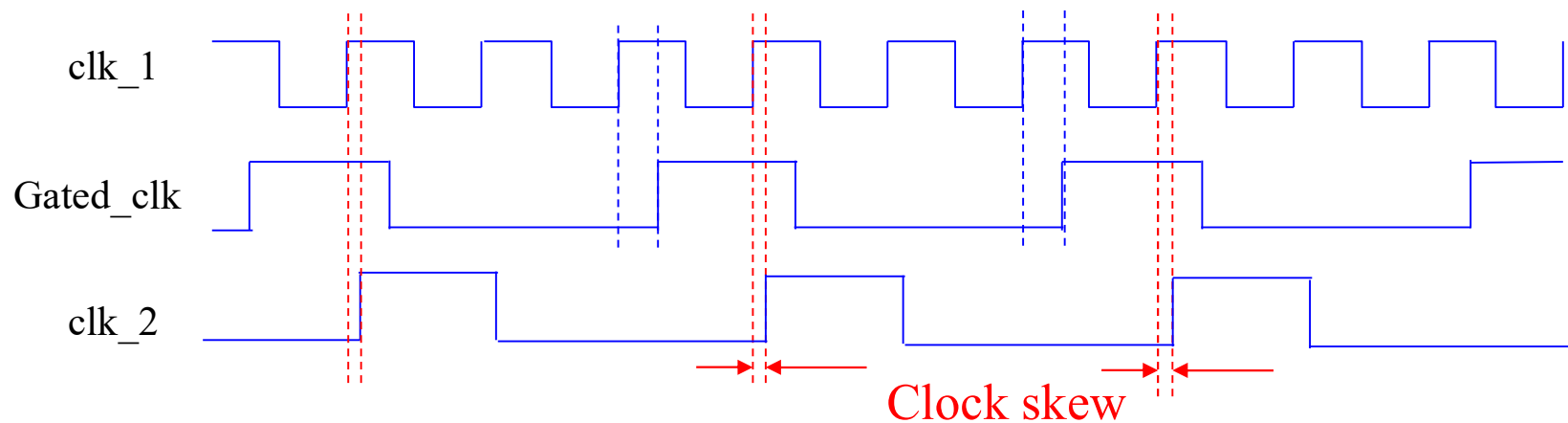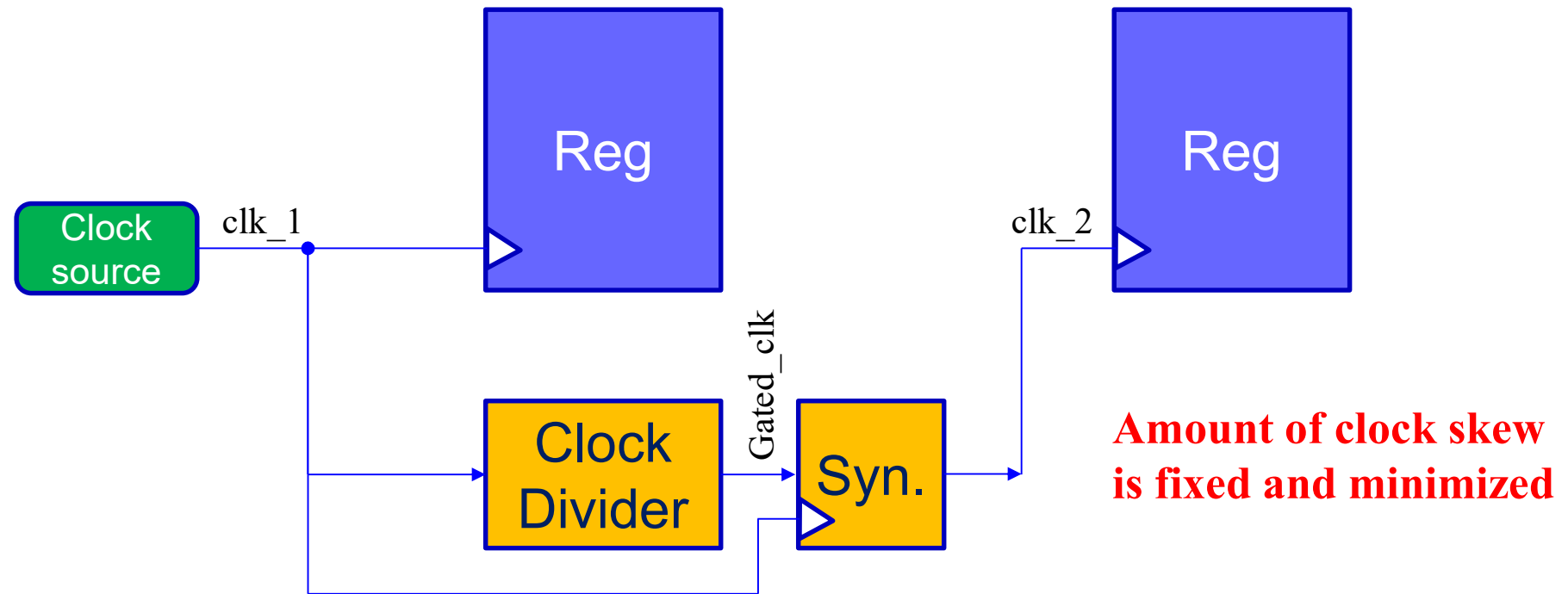

Ring Counter

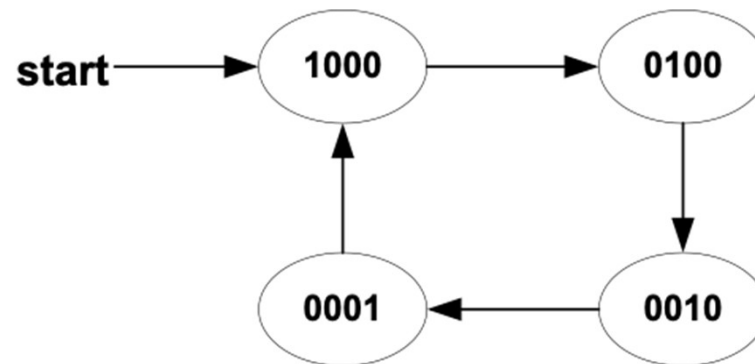- A ring counter is a circular shifter with only FF being set at any time



Current				Next			
1	0	0	0	0	1	0	0
0	1	0	0	0	0	1	0
0	0	1	0	0	0	0	1
0	0	0	1	1	0	0	0
all other inputs				X			


$D3 = Q0$
 $D2 = Q3$
 $D1 = Q2$
 $D0 = Q1$

Ring Counter – Design Alternative

- A ring counter is a circular shift register with only one FF being set at any time


w_1	w_0	P_0	P_1	P_2	P_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

functional table of 2×4 Decoder

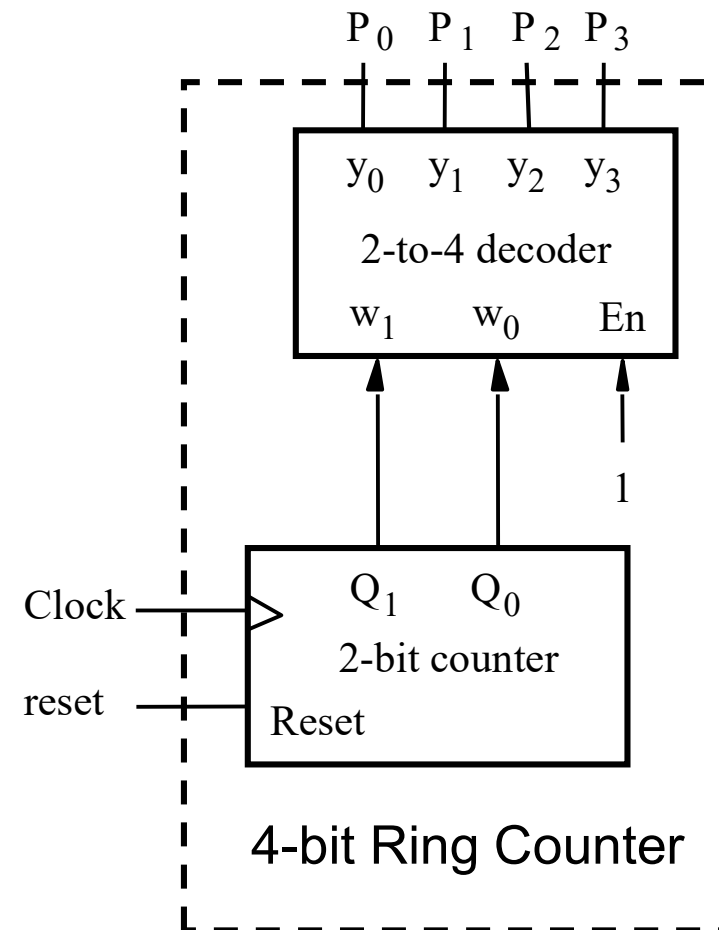

Ring Counter Example: Light Sequencer

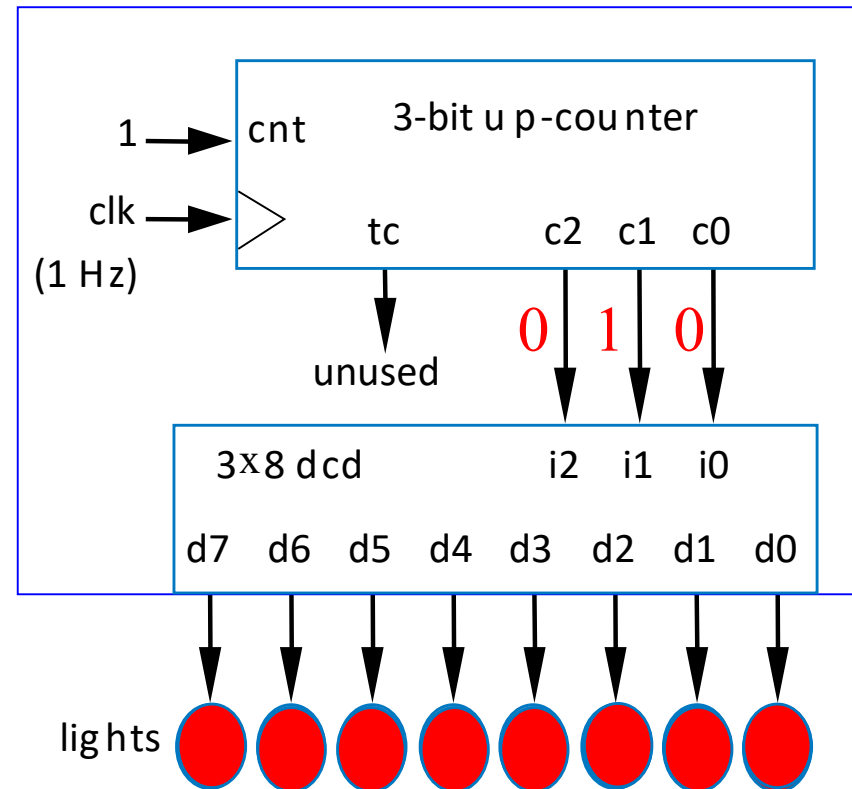- Illuminate 8 lights from right to left, one at a time, one per second



Johnson Counter

- Counting sequence

1000 → 1100 → 1110 → 1111 → 0111 → 0011 → 0001 → 0000 → ...

- In each state transition,
 - less state transition effort
 - but less counting state too


BCD Counter

- A counter doesn't have to follow through the entire counting sequence
- Example: BCD (Binary Coded Decimal) counter

Q3	Q2	Q1	Q0	Q3 ⁺	Q2 ⁺	Q1 ⁺	Q0 ⁺
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	X			
		.					
		.					
		.		X			
1	1	1	1				

2-Digit BCD Counter

- BCD: Binary Coded Decimal


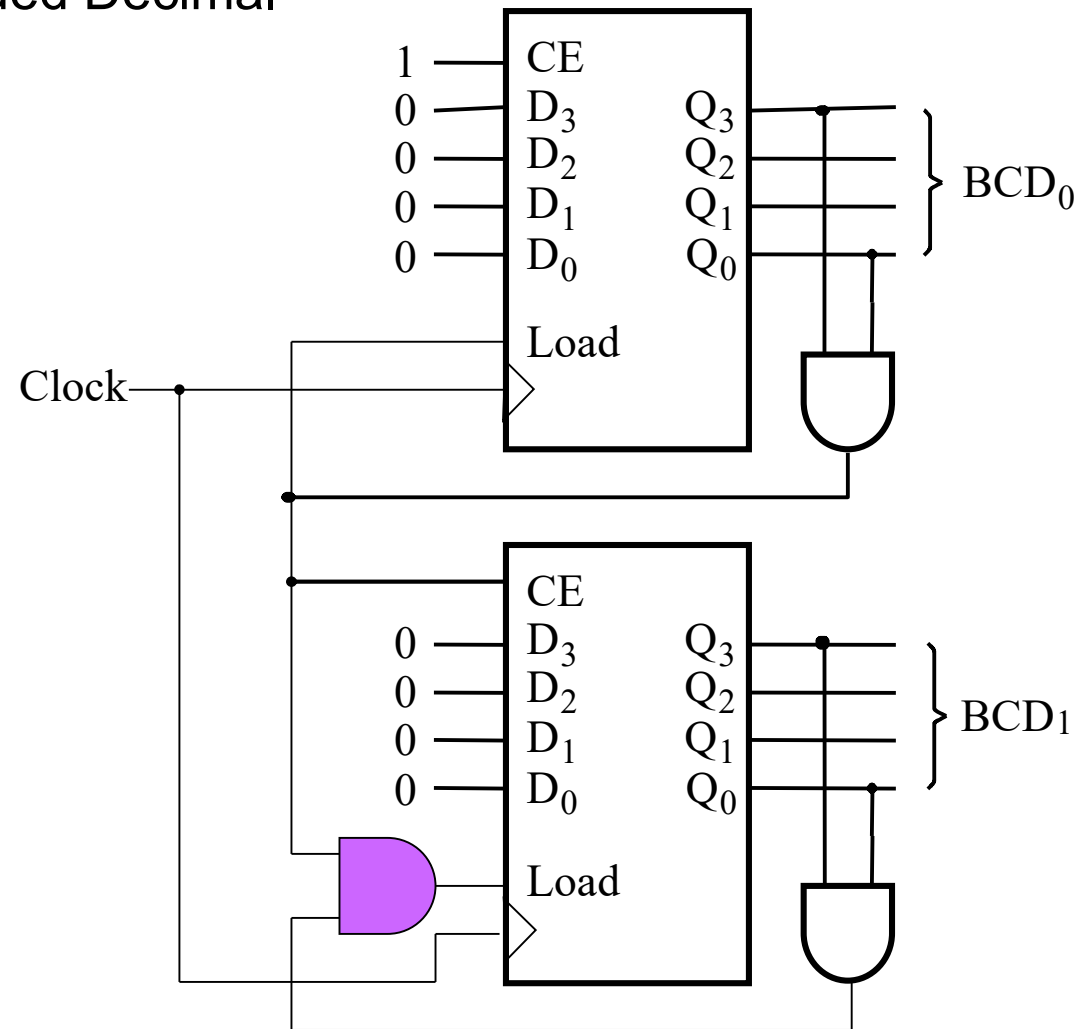


Alternative Design of Binary Counter

- Higher level (Register Transfer Level – RTL) design with combinational and sequential building blocks




- Example: up counter

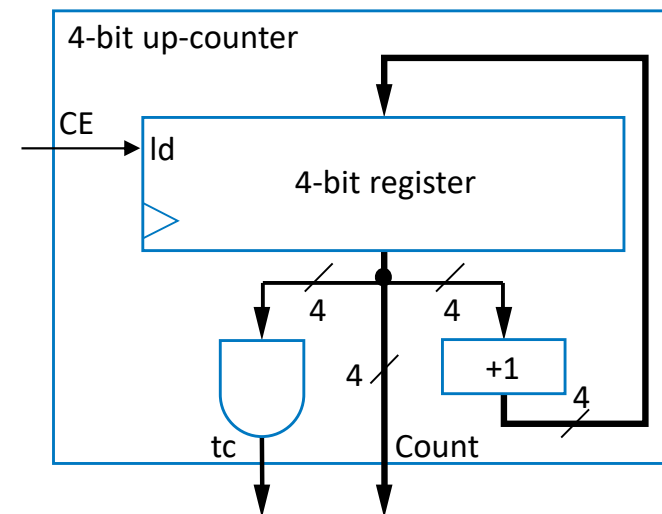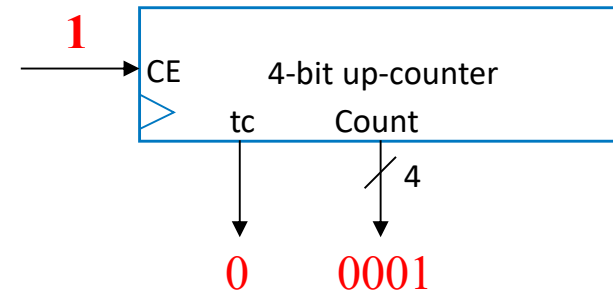

Down-Counter


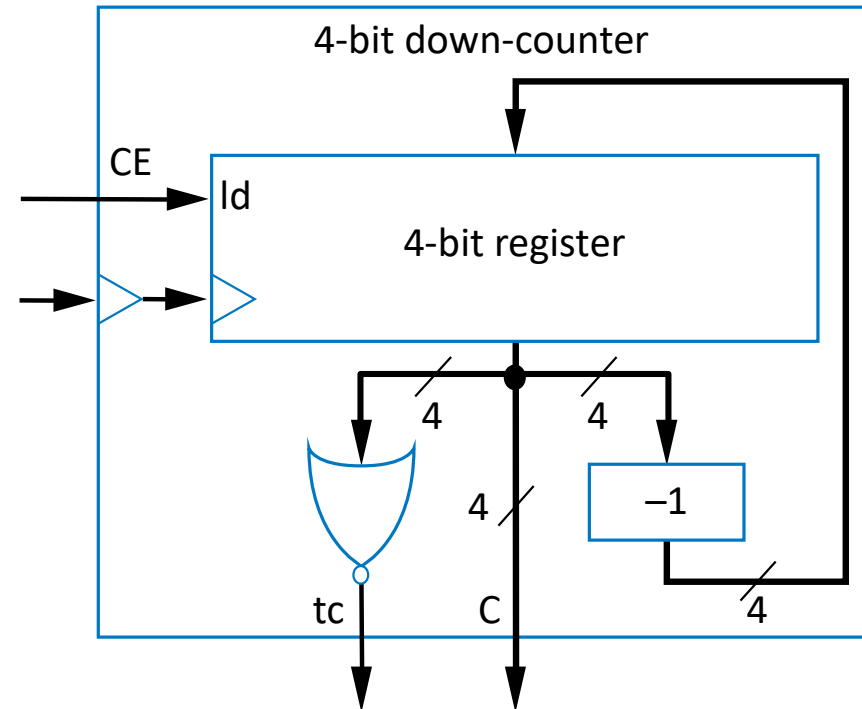
- 4-bit down-counter
 - Terminal count is 0000
 - Use NOR gate for tc
 - Need decrementer (-1)



Up/Down-Counter


- Can count either up or down

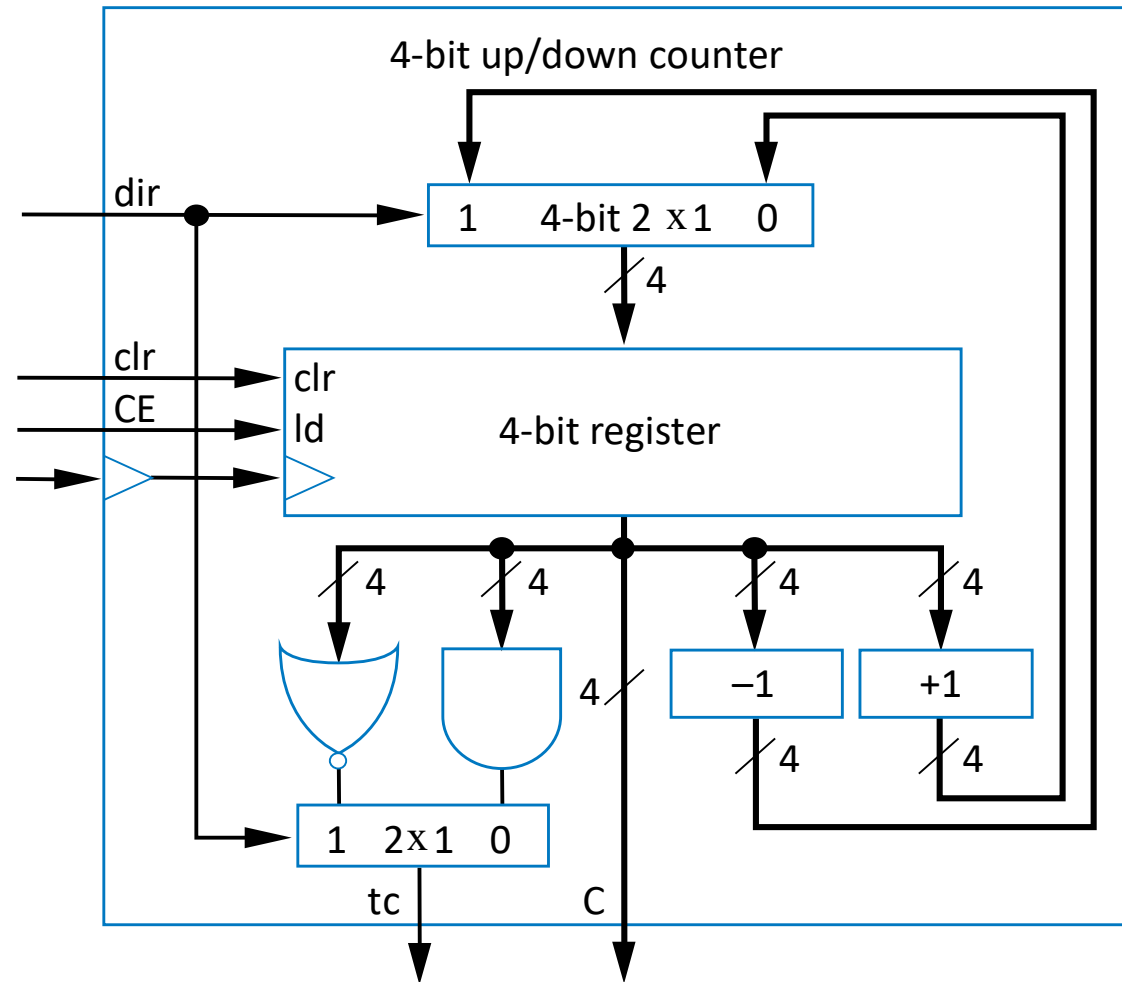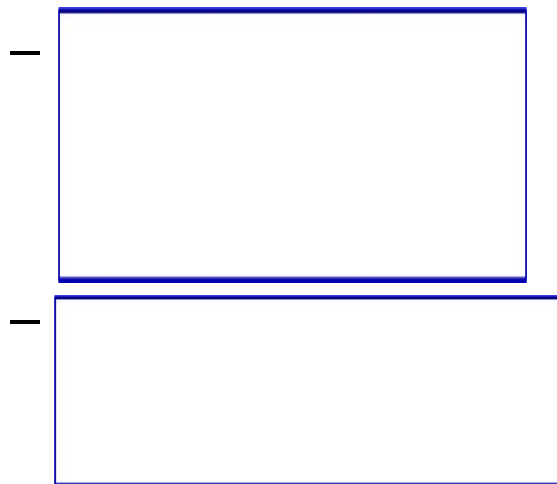- Includes both incrementer and decrementer




Alternative Design of Counter with Control

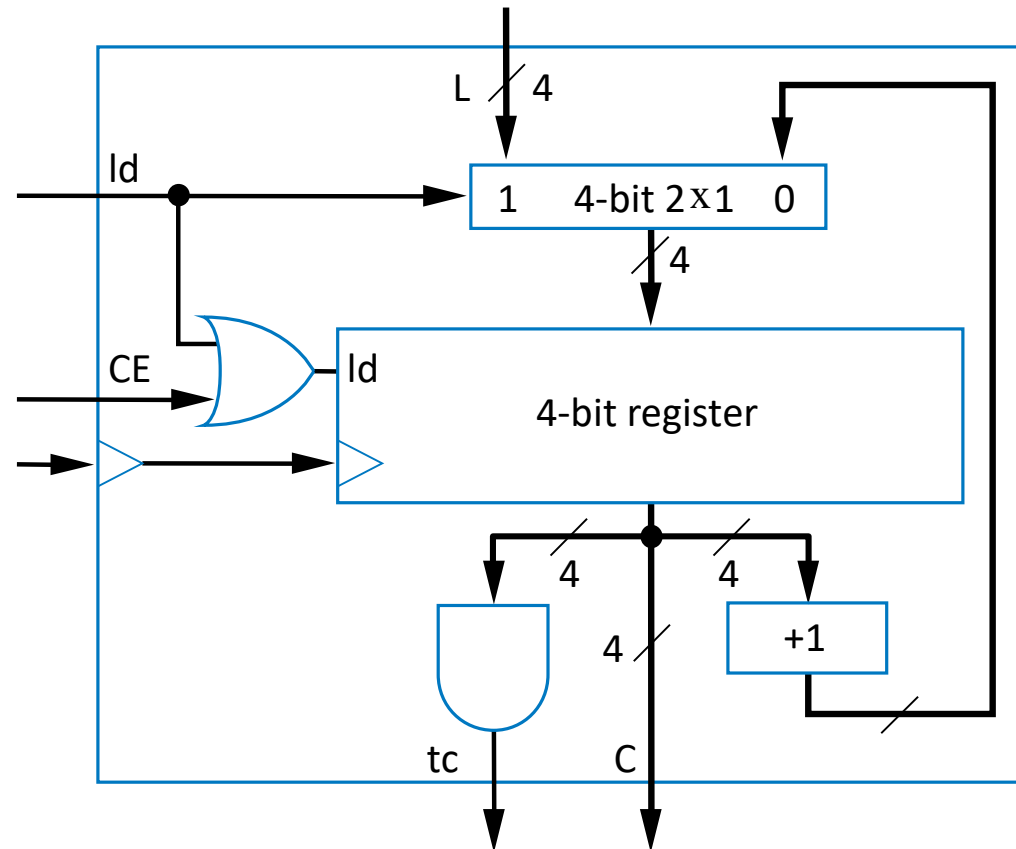- Up-counter that can be loaded with external value
 - Designed using 2x1 mux
 - Id input selects incremented value or external value
 - Load the internal register when loading external value or when counting



Counter Application – Timer

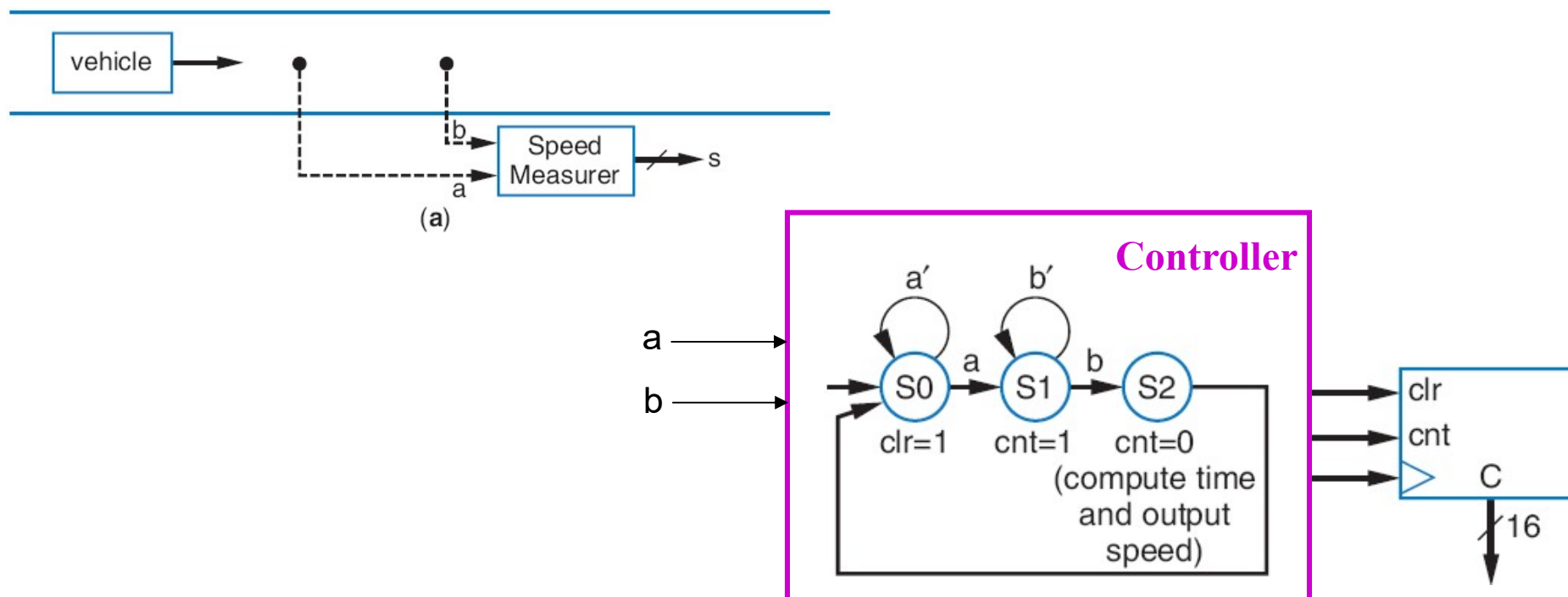- A type of counter used to measure time
 - If we know the counter's clock frequency and the count, we know the time that's been counted
- Example: Compute car's speed using two sensors
 - First sensor (a) clears and starts timer, second sensor (b) stops timer
 - Assuming clock of 1kHz, timer output represents time to travel between sensors. Knowing the distance, we can compute speed



Summary

- What essentially does a counter do?
- How to design a synchronous counter w/ FFs and gates?
- Verilog modeling of counters
- How to integrate control signals into a counter (w/ MUX)?
- Test bench, test plan, and UUT
- Clock divider as an important application of counter
- What is clock skew? How to reduce it? (w/ synchronizer)
- How to put together a counter with building blocks?